



Signals and Systems Laplace Transform and Its Applications

Student: Ali Abbasi (ID: 9531503)


Course Instructors: Dr. M Shahraki, Dr. M Mehrjoo

Course Number: 20 14 255

Faculty of Electrical and Computer Engineering,
University of Sistan and Baluchestan, Zahedan, Iran


Note: All trademarks, logos, service marks displayed, and software used to make this video are the trade mark of their respective company.

Frequency Range

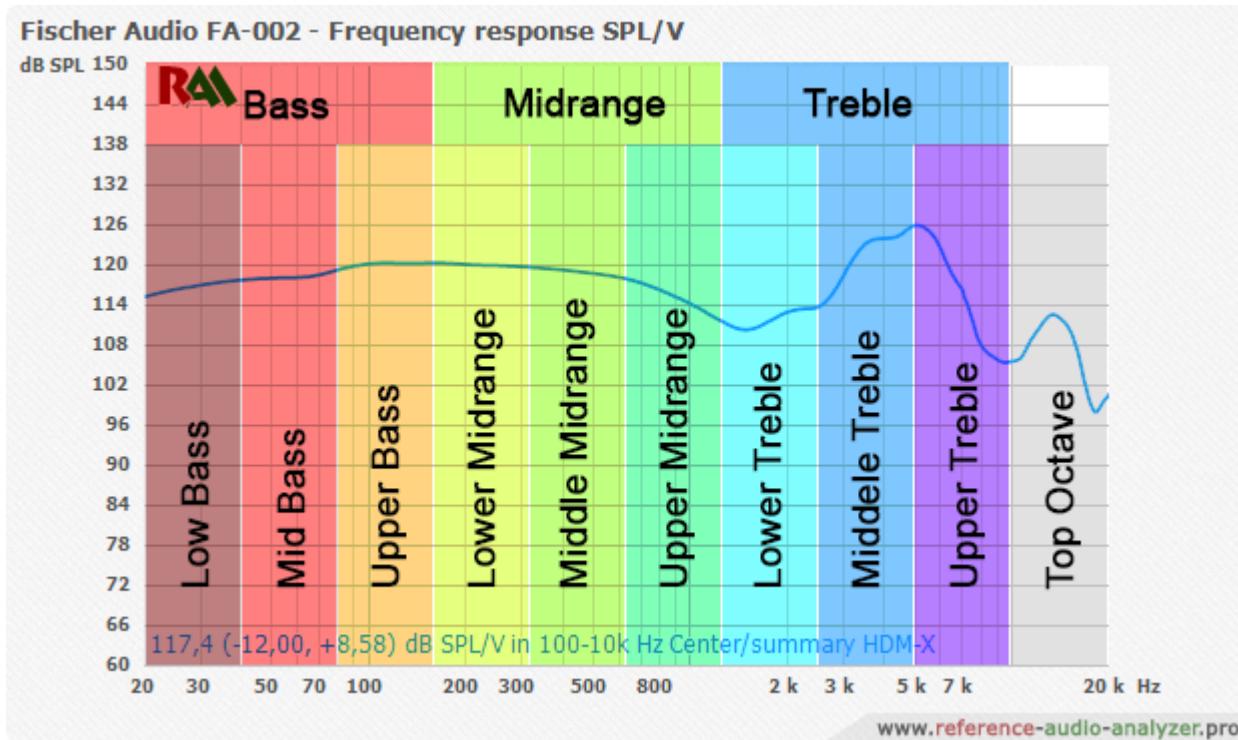


Note: This slide has been used in assignment 9 to present applications of Fourier analysis.

Audio Systems with Multiple Speakers

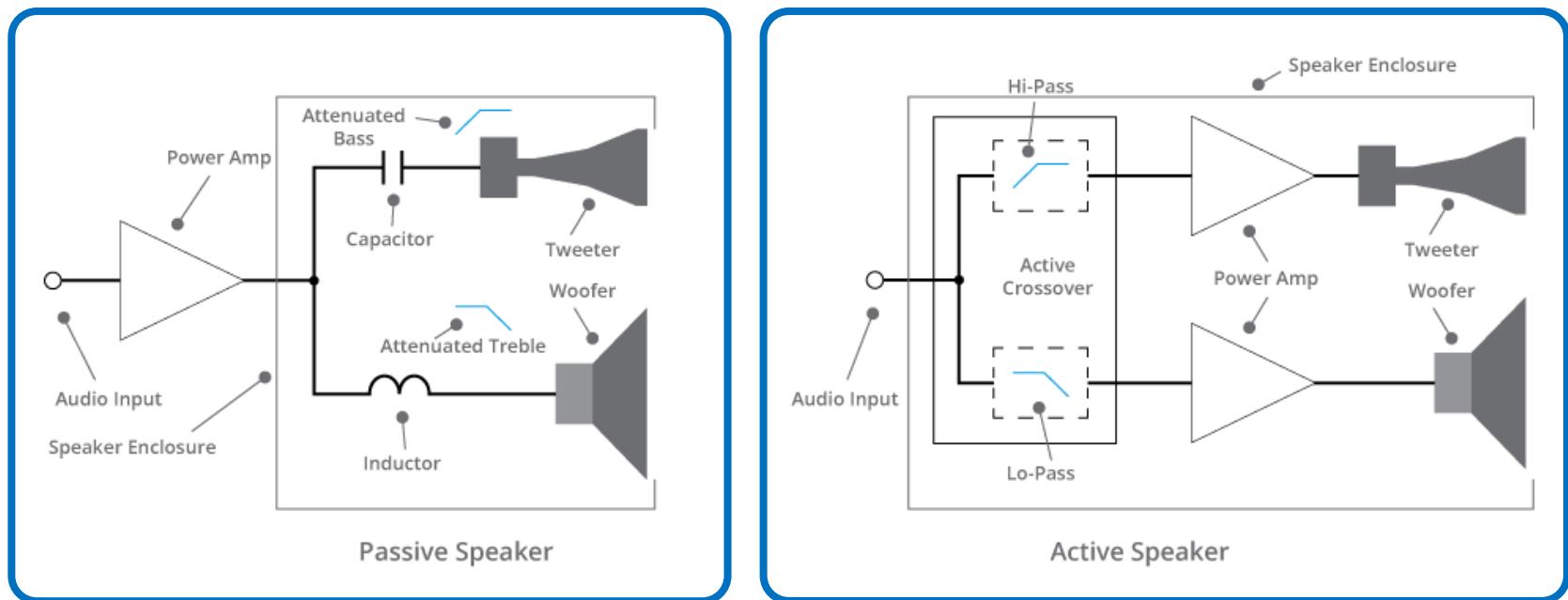


Picture Source: <https://www.bhphotovideo.com/explora/amp/audio/tips-and-solutions/what-about-all-those-speaker-specs>
Note: This slide has been used in assignment 9 to present applications of Fourier analysis.

Filters Circuits

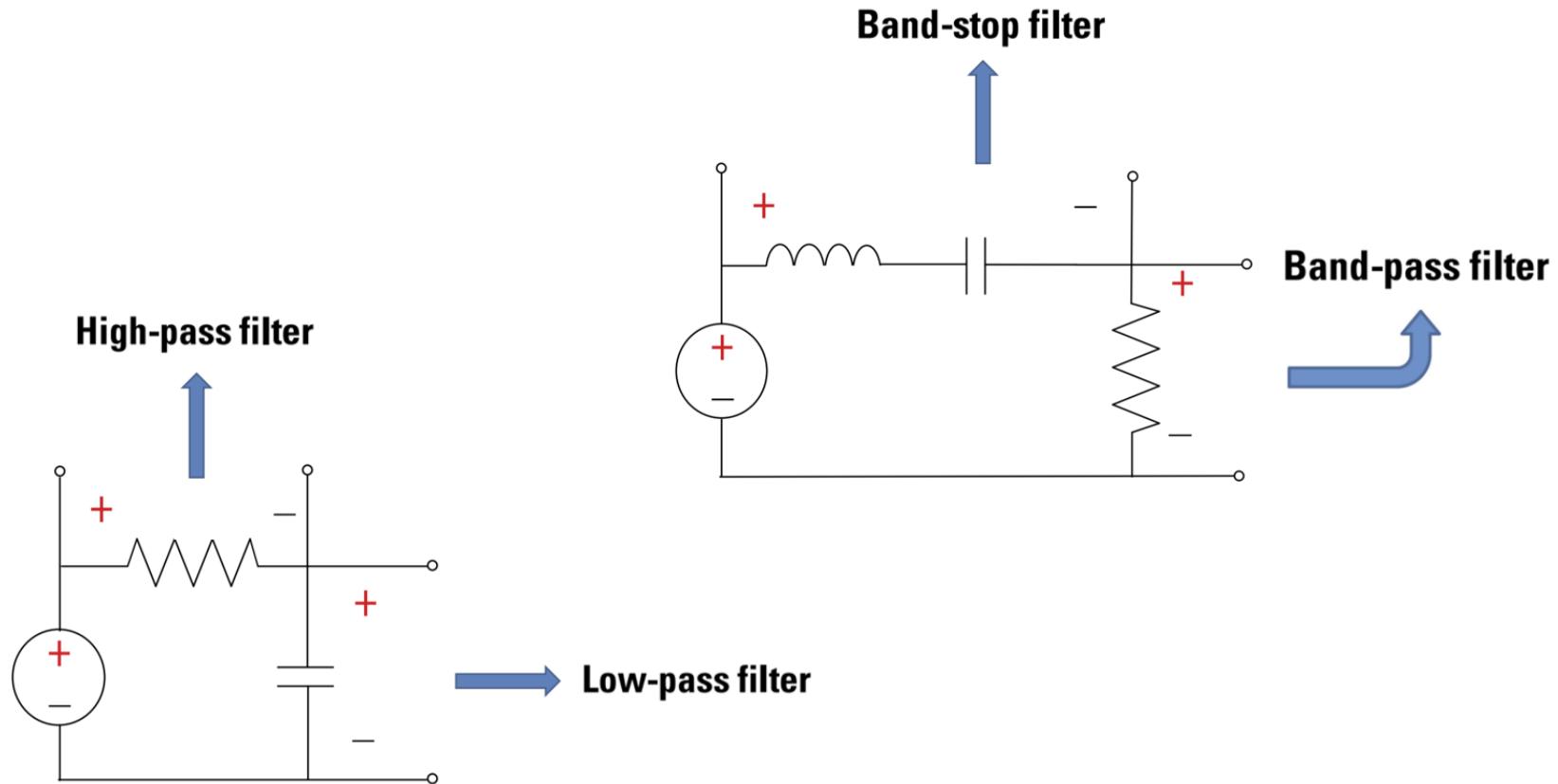

Low-pass Filter Analysis

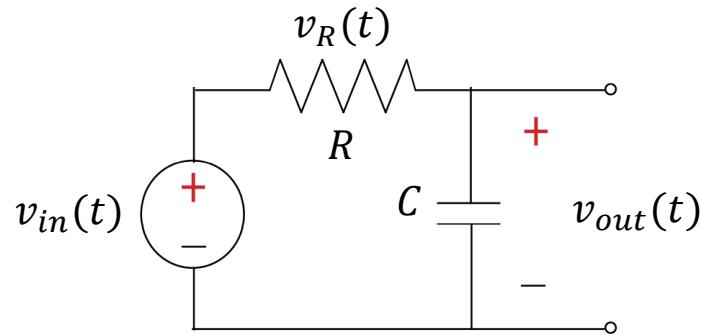

All initial conditions are zero.

$$v_{in}(t) = v_R(t) + v_{out}(t)$$

$$v_{in}(t) = Ri(t) + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

$$v_{in}(t) = RC \frac{dv_{out}(t)}{dt} + \frac{1}{C} \int_{-\infty}^t C \frac{dv_{out}(\tau)}{dt} d\tau$$

$$v_{in}(t) = RC \frac{dv_{out}(t)}{dt} + v_{out}(t)$$

Low-pass Filter Analysis (cont.)

$$v_{in}(t) = RC \frac{dv_{out}(t)}{dt} + v_{out}(t)$$

Laplace 

$$V_{in}(s) = RCsV_{out}(s) + V_{out}(s)$$

$$V_{in}(s) = V_{out}(s)(RCs + 1)$$

$$v_{out}(t) = v_{in}(t)(1 - e^{-\frac{1}{RC}t})$$


Laplace⁻¹ 

$$V_{out}(s) = \frac{1}{RC} \left(\frac{1}{s + \frac{1}{RC}} \right) V_{in}(s)$$


Devices in S-Domain

Device	Time – Domain	S – Domain			Impedance (with zero initial condition)
		Voltage	Current		
IVS	$v_S(t)$	$V_S(s)$	–	–	–
ICS	$i_S(t)$	–	$I_S(s)$	–	–
VCVS	$v_2(t) = \mu v_1(t)$	$V_2(s) = \mu V_1(s)$	–	–	–
VCCS	$i_2(t) = g v_1(t)$	–	$I_2(s) = g V_1(s)$	–	–
CCVS	$v_2(t) = r i_1(t)$	$V_2(s) = r I_1(s)$	–	–	–
CCCS	$i_2(t) = \beta i_1(t)$	–	$I_2(s) = \beta I_1(s)$	–	–
Resistor	$v_R(t) = R i_R(t)$	$V_R(s) = R I_R(s)$	$I_R(s) = \left(\frac{1}{R}\right) V_R(s)$	$Z_R(s) = R$	
Capacitor	$v_C(t) = \int_0^t i_C(\tau) d\tau$	$V_C(s) = \frac{1}{sC} I_C(s) + \frac{v_{c(0)}}{s}$	$I_C(s) = (sC)V_C(s) - C v_c(0)$	$Z_C(s) = \frac{1}{sC}$	
Inductor	$v_L(t) = L \frac{di_L(t)}{dt}$	$V_L(s) = sLI_L(s) - Li_L(0)$	$I_L(s) = \left(\frac{1}{sL}\right) V_L(s) + \frac{i_L(0)}{s}$	$Z_L(s) = sL$	

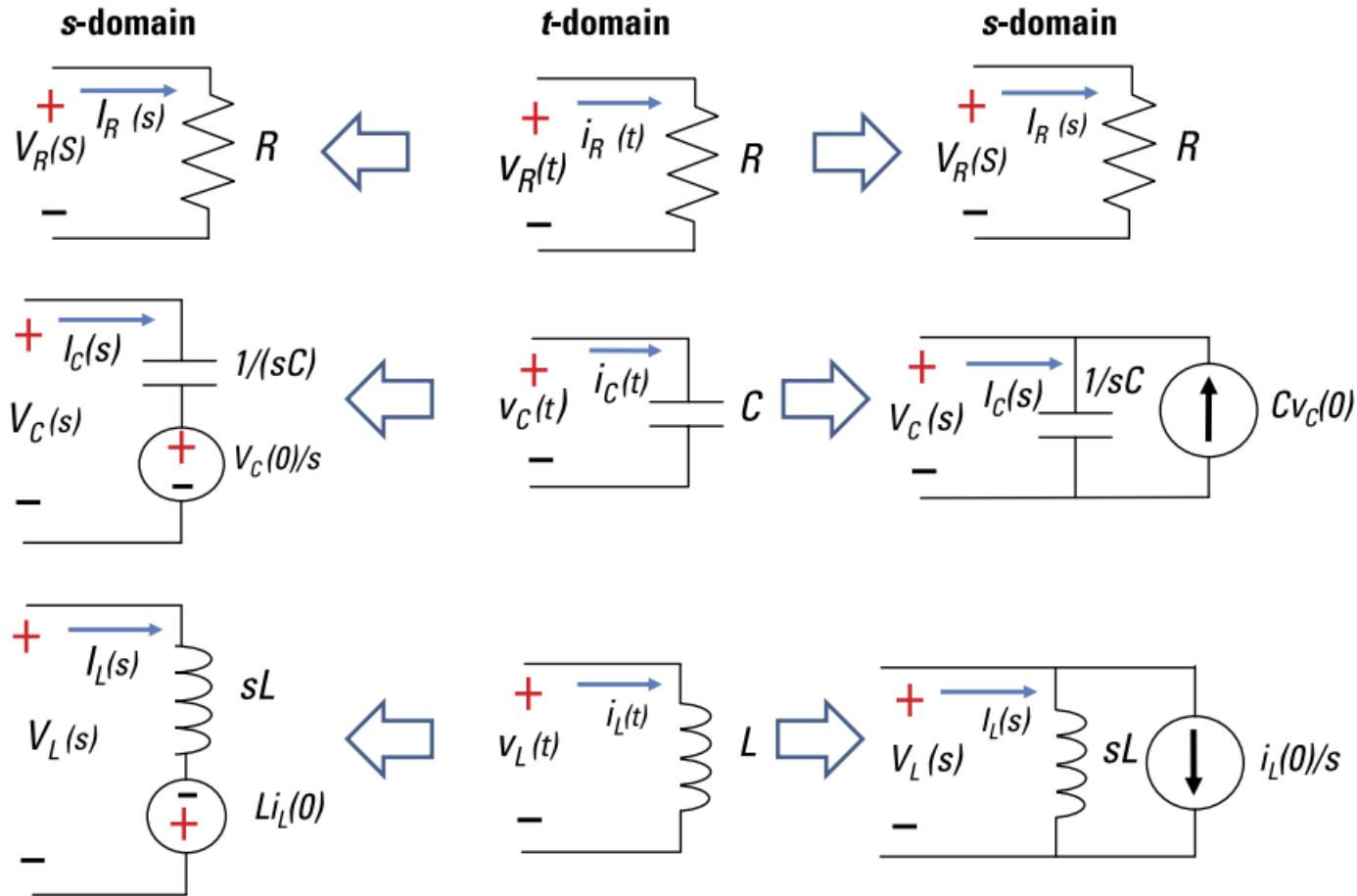S-Domain Thévenin's and Norton's Equivalent for Passive Elements



Band-pass Filter: S-Domain Analysis

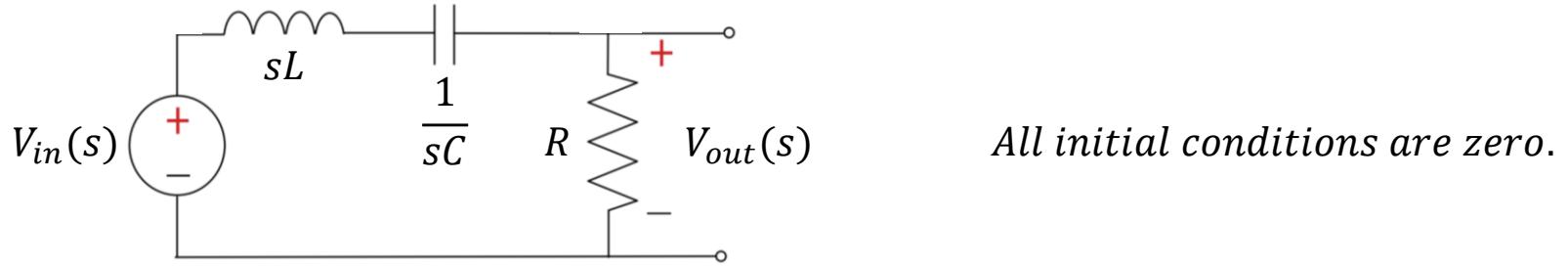

All initial conditions are zero.

$$V_{out}(s) = \left(\frac{R}{sL + \frac{1}{sC} + R} \right) V_{in}(s)$$

$$T(s) = \frac{V_{out}(s)}{V_{in}(s)} = \left(\frac{R}{L} \right) \frac{s}{\left[s^2 + \left(\frac{R}{L} \right) s + \frac{1}{LC} \right]}$$

Band-pass Filter: S-Domain Analysis (cont.)


$$s = j\omega \rightarrow T(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \left(\frac{R}{L}\right) \frac{j\omega}{[(j\omega)^2 + \left(\frac{R}{L}\right)s + \frac{1}{LC}]} = \left(\frac{R}{L}\right) \frac{j\omega}{\left[\left(\frac{1}{LC} - \omega^2\right) + \left(\frac{R}{L}\right)j\omega\right]}$$

$$\frac{1}{LC} - \omega^2 = 0 \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\frac{1}{LC} - \omega^2 = \pm \frac{R}{L}\omega \rightarrow \omega^2 \pm \frac{R}{L}\omega - \frac{1}{LC} = 0 \rightarrow \begin{cases} \omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \\ \omega_{c2} = +\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \end{cases}$$

$$Band_width = \omega_{c2} - \omega_{c1} = \frac{R}{L} \quad and \quad Q_factor = \frac{\omega_0}{BandWidth} = \frac{1/\sqrt{LC}}{R/L} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Band-pass Filter as a System

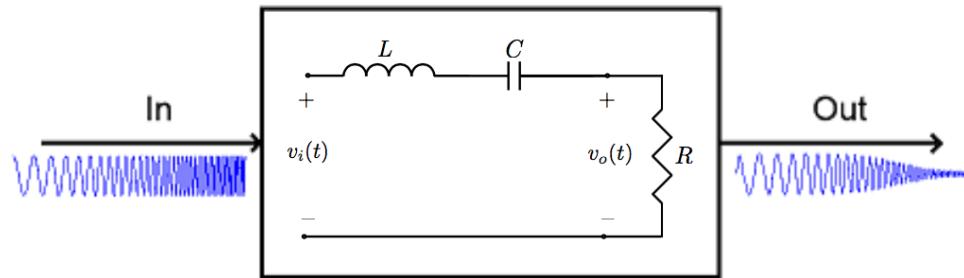

- For a band-pass filter (all initial conditions are zero):

$$T(s) = \frac{A_0 2\zeta \omega_0 s}{s^2 + 2\zeta \omega_0 s + \omega_0^2} = \frac{A_0 \frac{\omega_0}{Q} s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} = \frac{A_0 B s}{s^2 + Bs + \omega_0^2}$$


A_0 : Midband Gain

ω_0 : Resonant Frequency

ζ : Damping Coefficient

Q : Quality Factor

Control Systems and S-Domain

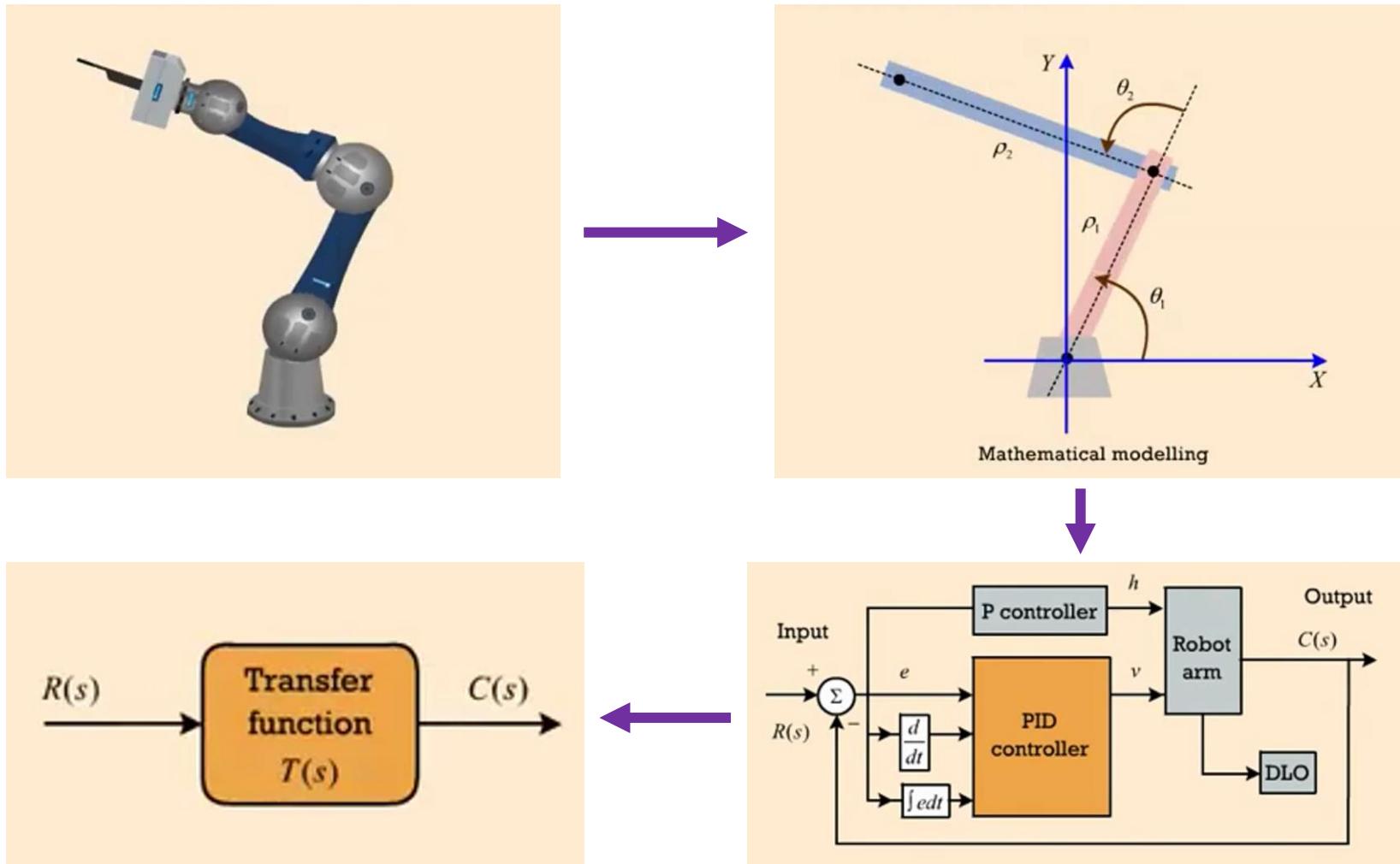


Picture Source: “Applications of Laplace Transform in Control Systems.”, “Mobile Tutor” channel on YouTube.

Control Systems and S-Domain (cont.)

- Help in solving differential equations of higher orders and evaluating system output.
- Gain Factor K:


$$T(s) = \frac{1}{As^2 + Bs + C} \xrightarrow{\text{Magnitude Amplification}} T(s) = K \frac{1}{As^2 + Bs + C}$$

- Nyquist Diagram

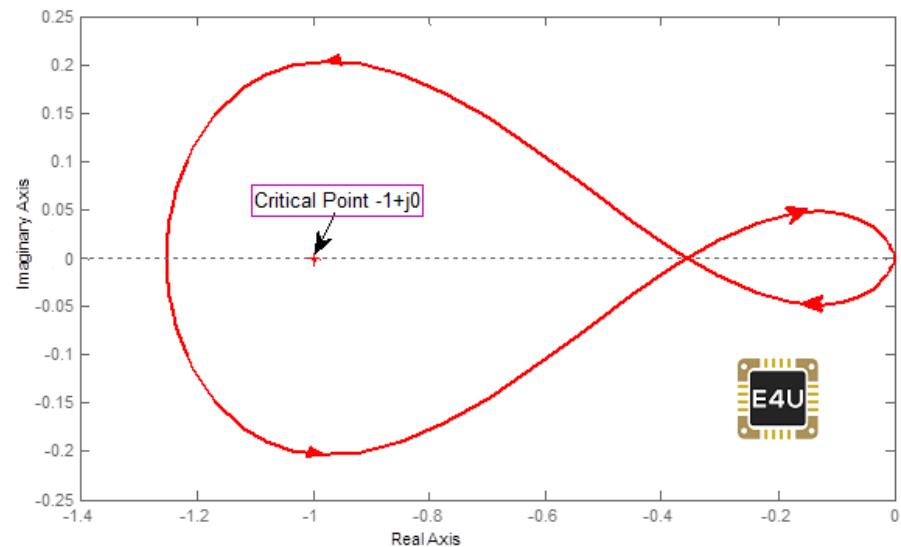


Control Systems and S-Domain (cont.)

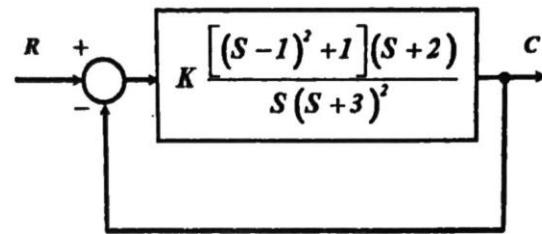۱- محدودهای برای K طوری بدست آورید که تنها دو قطب حلقه بسته‌ی سیستم زیر بین خطوط $\sigma = 0$ و $\sigma = -I$ قرار بگیرند. حداقل مقدار خطای حالت دائم به ورودی شیب واحد و نیز کمترین زمان نشست دو درصد این سیستم در پاسخ به ورودی پله در محدوده‌ی تعیین شده تقریباً چقدر است؟



Control Systems and S-Domain (cont.)

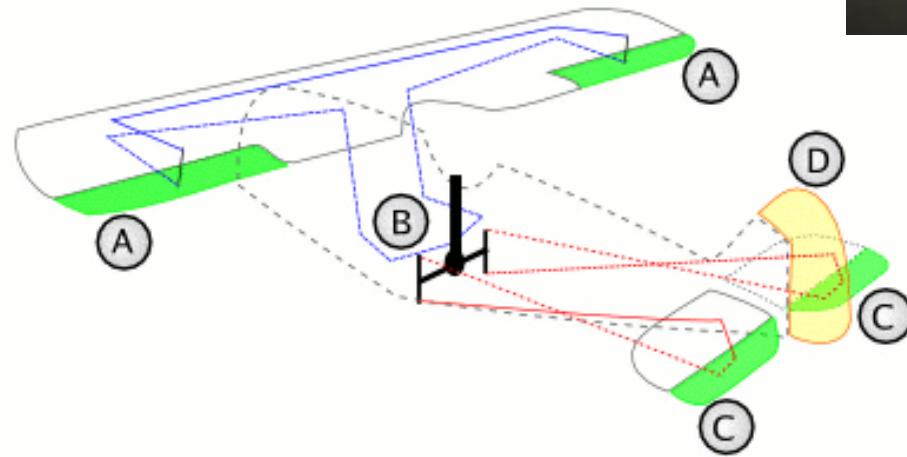- Faster forecasting of the outputs of a system.





The END!